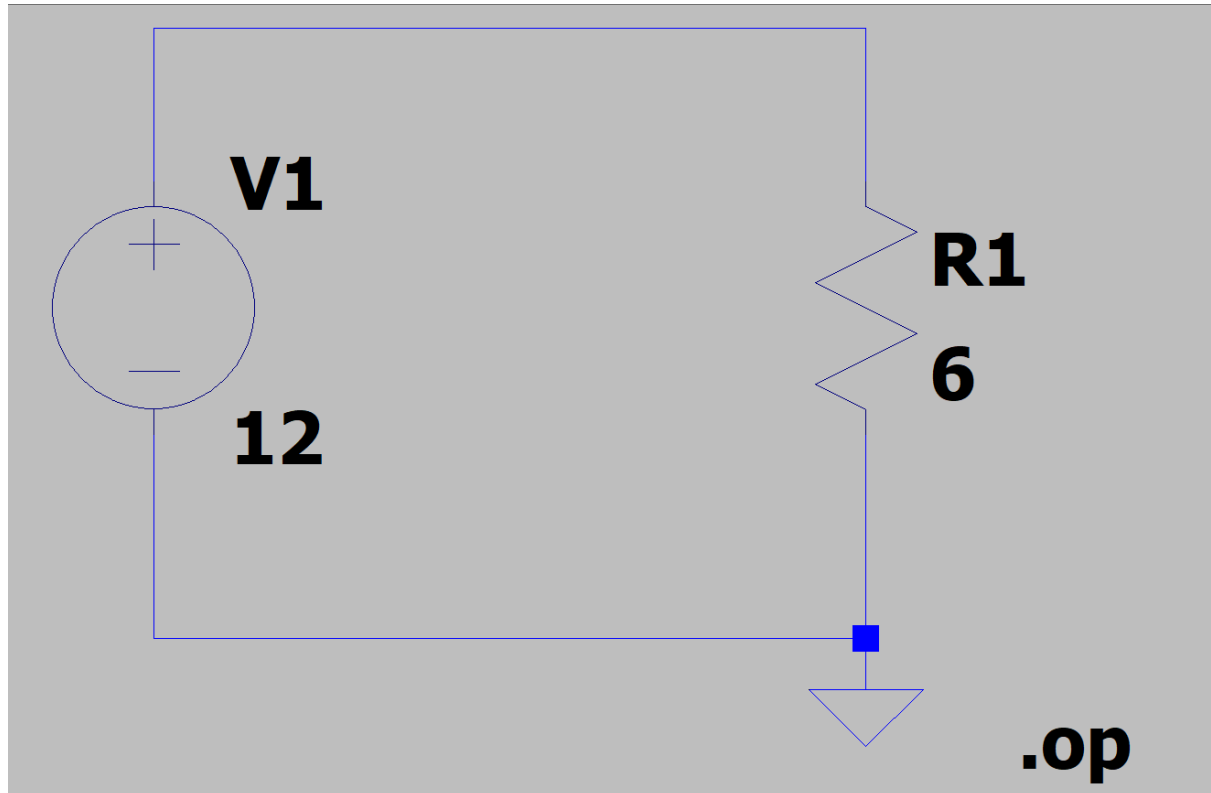


SIMPLE RESISTOR CIRCUIT

CIRCUIT DIAGRAM



PRINCIPLE: Ohm's Law.

OUTPUT:

--- Operating Point ---

V(n001) :	12	voltage
I(R1) :	2	device_current
I(V1) :	-2	device_current